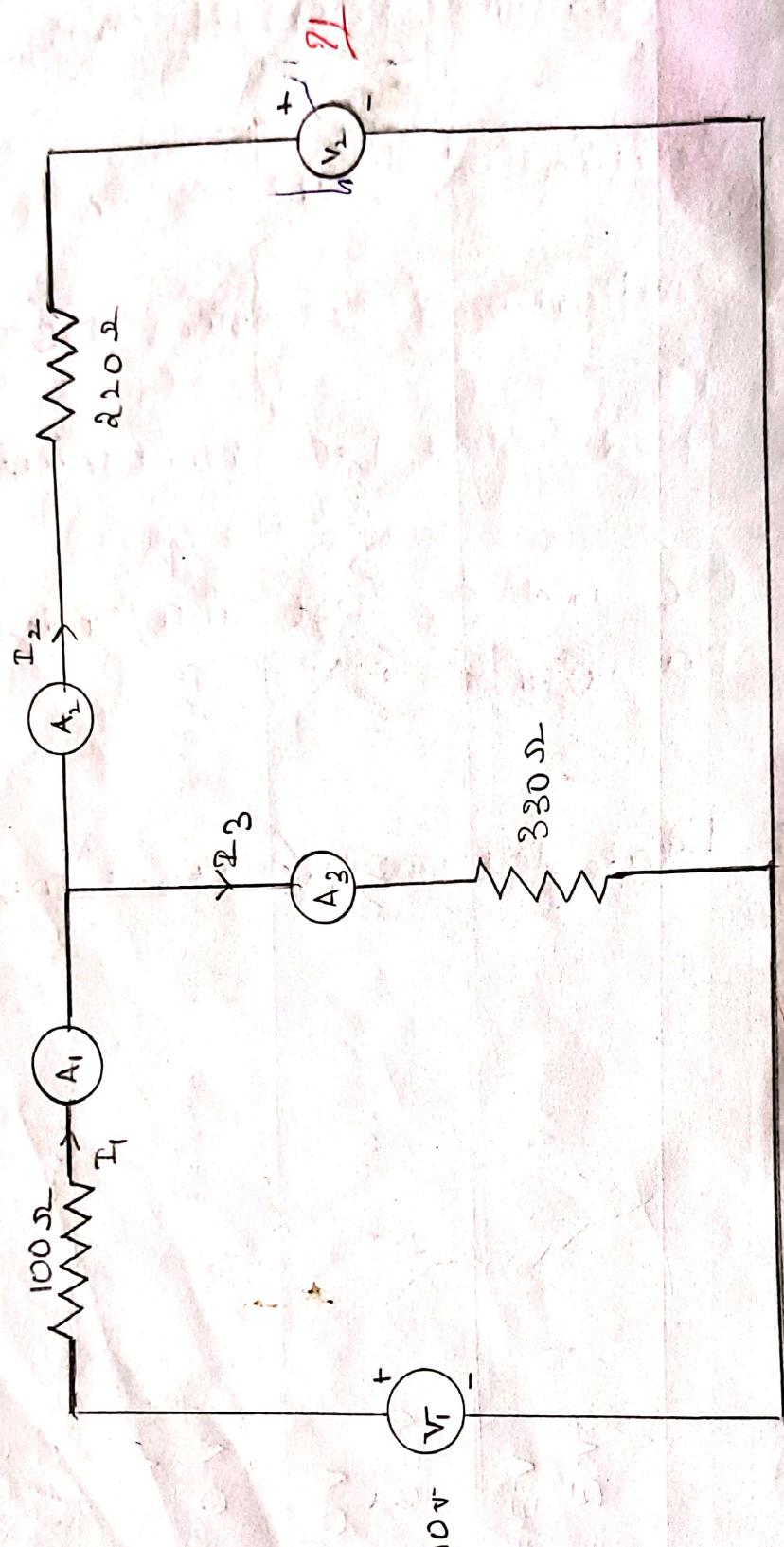


## CIRCUIT DIAGRAM



# Experiment - I Superposition Theorem

Aim: To Verify superposition Theorem

- Apparatus:
1. Physitechs superposition Theorem trainer kit
  2. Milli Ammeter (0-20mA)
  3. Connecting wires

## Procedure:

1. Switch on the Physitechs Superposition theorem trainer kit.
2. In trainer two power supplies are present One is variable (0-12V) and another is fixed 5V.
3. Connect the 0-12V supply to  $V_1$  and 5V supply to  $V_2$  terminal
4. Connect three milli ammeters to  $I_1$ ,  $I_2$ ,  $I_3$
5. Note down the three current values, when the two supplies are connected.
6. Short the supply  $V_2$  and note down corresponding  $I_1$ ,  $I_2$  and  $I_3$  readings due to voltage source  $V_1$ .
7. Verify the superposition theorem by using  $I_m$ .

Theoretical		Practical		
Source Voltages		T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
V <sub>1</sub> = 5 V	V <sub>2</sub> = 0 V	12.9 mA	16.8 mA	3.9 mA
V <sub>1</sub> = 0 V	V <sub>2</sub> = 5 V	12.9 mA	16.8 mA	3.9 mA
V <sub>1</sub> = 5 V	V <sub>2</sub> = 5 V	8.6 mA	12.6 mA	3.79 mA
V <sub>1</sub> = 0 V	V <sub>2</sub> = 0 V	20.9	12.79	8.53

8. Repeat the same procedure for another values of voltage (for ex: 5V, 8V, 12V).

Calculation:-

$$\frac{x-5}{100} + \frac{x-0}{220} + \frac{x-0}{330} = 0 \Rightarrow \frac{x-5}{100} = -\left(\frac{330x+220x}{330 \times 200}\right)$$


$$\frac{5-x}{10} = \frac{550}{33 \times 22} x \quad | = \frac{x-5}{100} \Rightarrow \frac{2.84-x}{100}$$

$$5-x = \frac{25x}{33} \quad = 0.216 \text{ mA}$$

$$\Rightarrow \frac{33x-5}{58} = x \quad S_1 = \frac{x}{220} = 0.84 \text{ mA}$$

$$x = 0.84$$
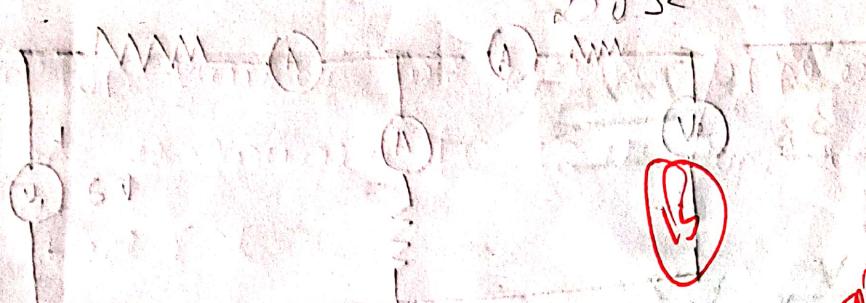
$$S_2 = \frac{x}{330} = 0.216 \text{ mA}$$



$$I_1 = 0.9 \text{ mA} \quad I_2 = 0.216 \text{ mA}$$

Result :- Superposition theorem is verified  
Practically and theoretically


$$I_1 = 0.9 \text{ mA}$$

$$x = 1.02 \text{ A} \quad I_{2g} = 3.9 \text{ mA}$$

$$I_2 = 16.8 \text{ mA}$$

Case ①: wenn  $V_1 = 5V$

$$V_2 = 0V$$

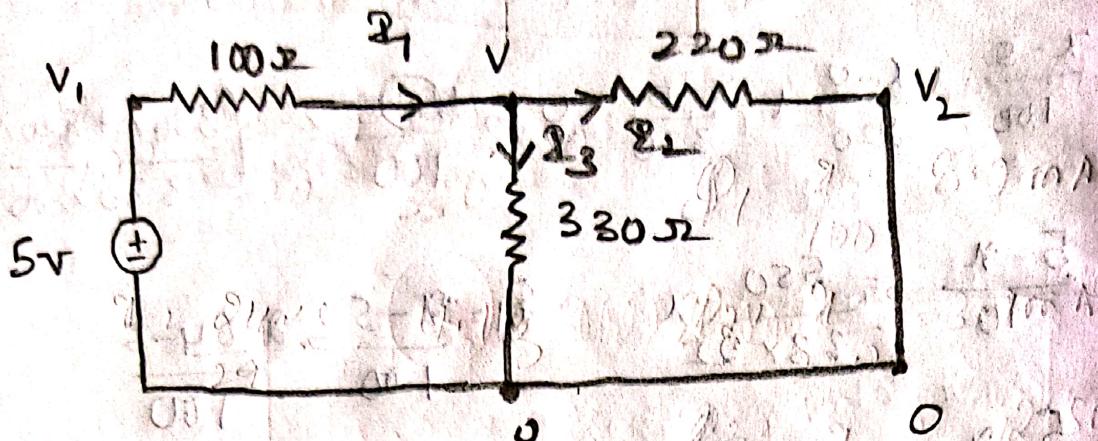

$$R_1 = R_3 + R_2$$

$$V_2 = 0$$

$$\frac{V_1 - 5}{100} = \frac{V}{330} + \frac{V - V_2}{220}$$

$$\textcircled{1} \times \frac{3}{220}$$


$$\frac{V_1 - 5}{10} = \frac{V}{33} + \frac{V - V_2}{22}$$

$$\frac{V_1 - 5}{10} = \frac{V}{33} + \frac{V}{22}$$

$$\frac{11V_1 - 55}{10} = \frac{2V + 3V}{6}$$

$$25V = 33V_1 - 165$$

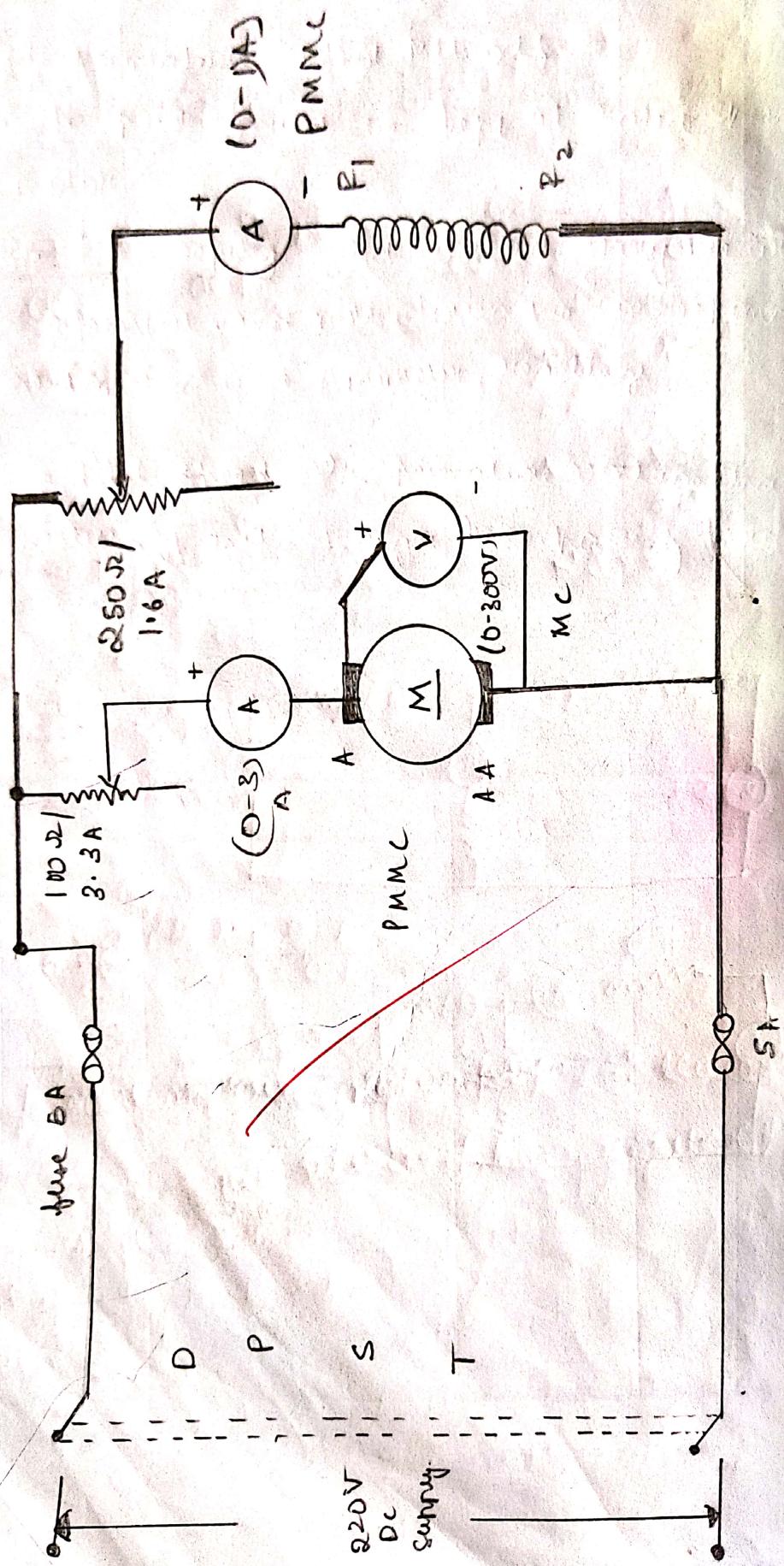Signature Diagram for speed control on DC shunt machine



## Experiment - II Speed Control of DC Shunt Motor

Aim:- To control the speed of the DC shunt motor

(i) Armature control and (ii) Field Flux Control

### Prerequisites

Apparatus Required:-

S.NO.	Name of the APP	Type	Range	No units
1	Ammeter	PMMC	(0-3)A (0-1)A	1 1
2	Voltmeter	PMMC	0-300V	1
3	Rheostat	Wire wound	250Ω / 100Ω / 3.3A	1 1
4	Tachometer	Digital	(0-9999) RPM	1
5	Fuse	TCC	SA	2
6	Connecting wires	-	-	few wires

- Procedure :-
1. Connect the Apparatus as per the circuit diagram.
  2. Switch on the power supply and close the D.P.S.T switch
  3. Initially the field rheostat should be min-

Observations:-

Ammeter control:

S.NO	Ammeter Current (A)	Speed N (RPM)	Field current (A)	Ammeter voltage (V)
1	$0.82 \times 2 = 1.64$	1500	0.55	216
2	$0.8 \times 2 = 1.60$	1400	0.55	200
3	$0.8 \times 2 = 1.60$	1300	0.55	190
4	$0.77 \times 2 = 1.54$	1200	0.55	174
5	$0.75 \times 2 = 1.5$	1100	0.55	160
6	$0.75 \times 2 = 1.5$	1000	0.55	150
7	$0.75 \times 2 = 1.5$	900	0.55	134

Field Flux control:

S.NO	Ammeter Current (A)	Speed N (RPM)	Field current	Ammeter voltage (V)
1	$0.83 \times 2 = 1.64$	1500	0.55	216
2	$0.84 \times 2 = 1.60$	1550	0.52	216
3	$0.85 \times 2 = 1.62$	1600	0.50	216
4	$0.85 \times 2 = 1.7$	1650	0.48	216
5	$0.85 \times 2 = 1.7$	1700	0.45	216.

E  
to Adjust field resistance of motor to increase the speed to the rated speed.

(i) :- Armature Control Method :

1. Speed should be kept at rated speed of the motor.
2. By keeping field constant vary the armature rheostat and note down the corresponding voltmeter and ammeter readings.
3. Plot speed v/s armature voltage characteristics. It is a straight line passing through origin.

(ii) :- Field Control Method :-

1. Speed should be kept at rated speed.
2. By keeping armature voltage constant, field is varied and corresponding voltmeter and ammeter readings are noted.
3. Plot Speed v/s Field current characteristics. It is a rectangular hyperbola.

Precautions :-  
1. Before the supply is turned on, the field rheostat should be at minimum position and armature rheostat at maximum resistance position.

2. Avoid loose connections

3. Avoid parallax error while noting the readings from ... mm

Results: Speed below rated speed can be obtained through alternative voltage control in speed above rated speed using field control method.

(15)

Now



1. First start the pump at rated speed.

2. Then decrease the pump speed by decreasing the field current. Now constant torque is maintained. The motor will run at different speeds with different torque.



3. If field current is reduced to half, then the speed will increase to double.

4. If field current is increased to double, then the speed will decrease to half.

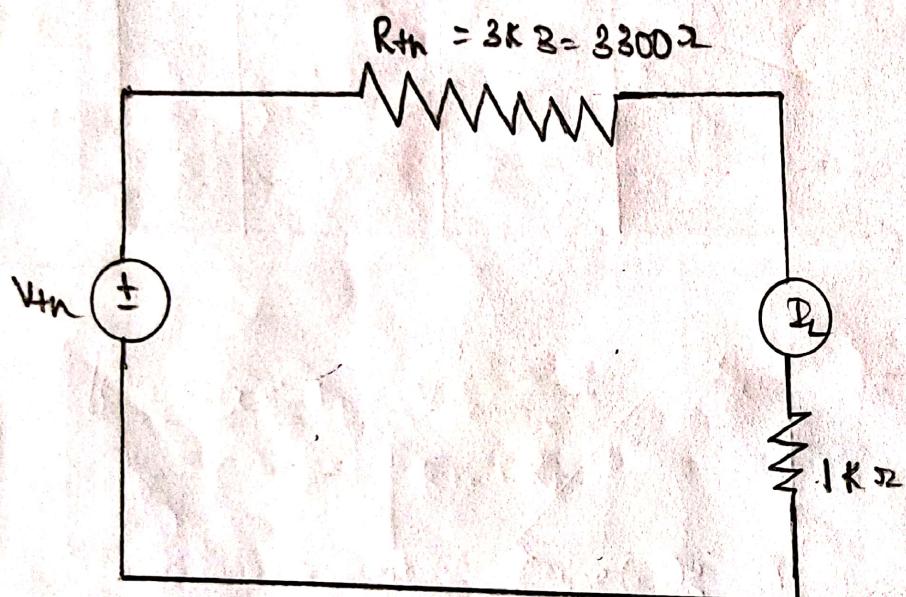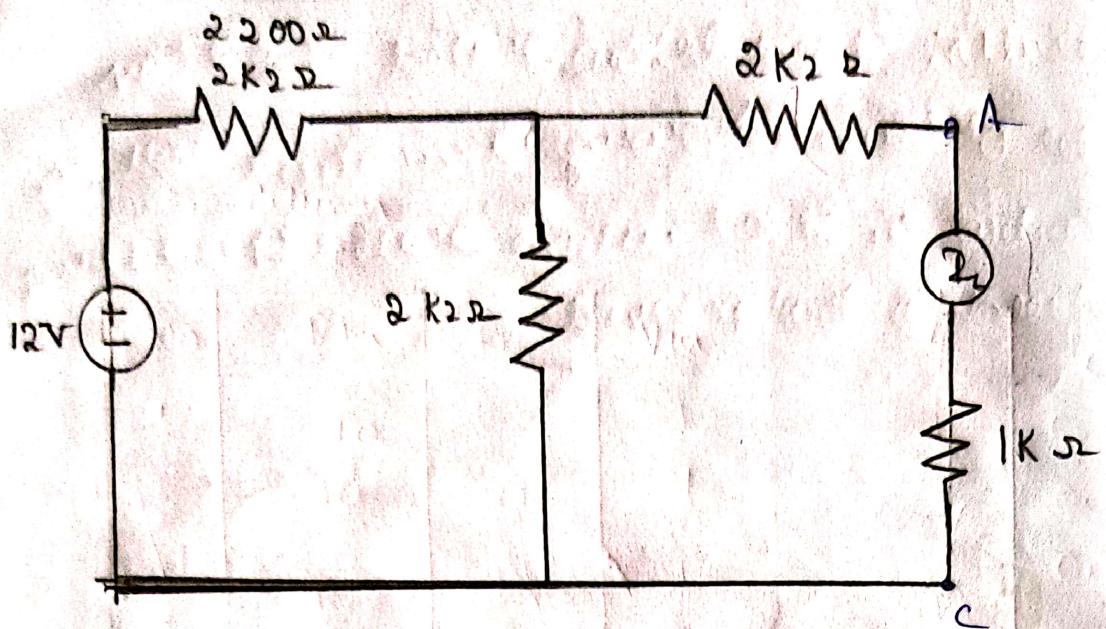5. If field current is increased to three times,

then the speed will decrease to one-third.





## Experiment-II) Thevenin's Theorem

Aim: To verify the Thevenin's Theorem.

- Apparatus:
1. PhysicsTechs. Thevenin's Theorem trainer kit
  2. Milli Ammeter (0-20mA)
  3. Voltmeter
  4. Connecting wires.

Procedure:-

1. Switch on the PhysicsTechs Thevenin's theorem trainer kit.
2. Connect the 0-12V supply to the V terminal.
3. Connect milli ammeter to the  $I_L$  terminal  
i.e., across A, B.
4. Note down the ammeter reading.
5. Connect the voltmeter across A and C terminals.
6. Note down the reading of  $V_{TH}$ .
7. Connect the  $V_{TH}$  supply to  $V_{TH}$  terminal of thevenin's equivalent circuit.
8. Connect Milli Ammeter to the  $I_L$  terminal  
i.e., across A, B of equivalent circuit.
9. Note down the ammeter reading.
10. Compare the  $I_L$  value of both the circuits.
11. Calculate theoretically by using the formula given.....

## Jabotovic Column

Example 1.4 of Saha and Bhattacharya

Revised by Prof. Dr. B. K. Bhattacharya

179

S.NO	R <sub>m</sub>	R <sub>L</sub>	V <sub>m</sub>	I <sub>L</sub>
1	10	5	12	0.80
2	10	10	12	0.60
3	10	15	12	0.48
4	10	20	12	0.40
5	10	25	12	0.34

minimum V<sub>m</sub> of 12V - 0.80A - 0.60A

formula:  $I_L = \frac{V_m}{R_m + R_L}$  when  $R_L < R_m$

Case 1 :-

$$I_L = \frac{12}{10+5} = 0.80A$$

Case 2 :-  $\frac{12}{10+10} = 0.60A$

Case 3 :-  $\frac{12}{20} = 0.60A$

Case 4 :-


$$I_L = \frac{12}{10+15} = 0.48A$$


Case 5 :-  $\frac{12}{30} = 0.40A$

Case 6 :-  $I_L = \frac{12}{10+25} = 0.34A$



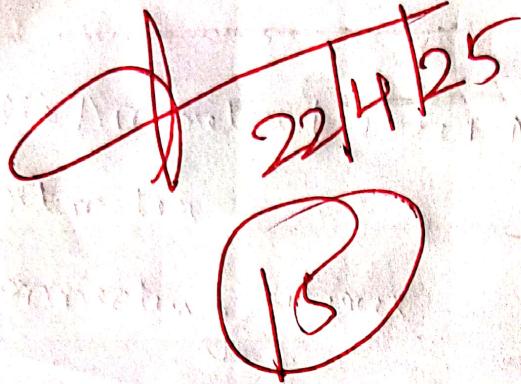~~Result: Hence thevenins theorem is verified  
theoretically and practically~~



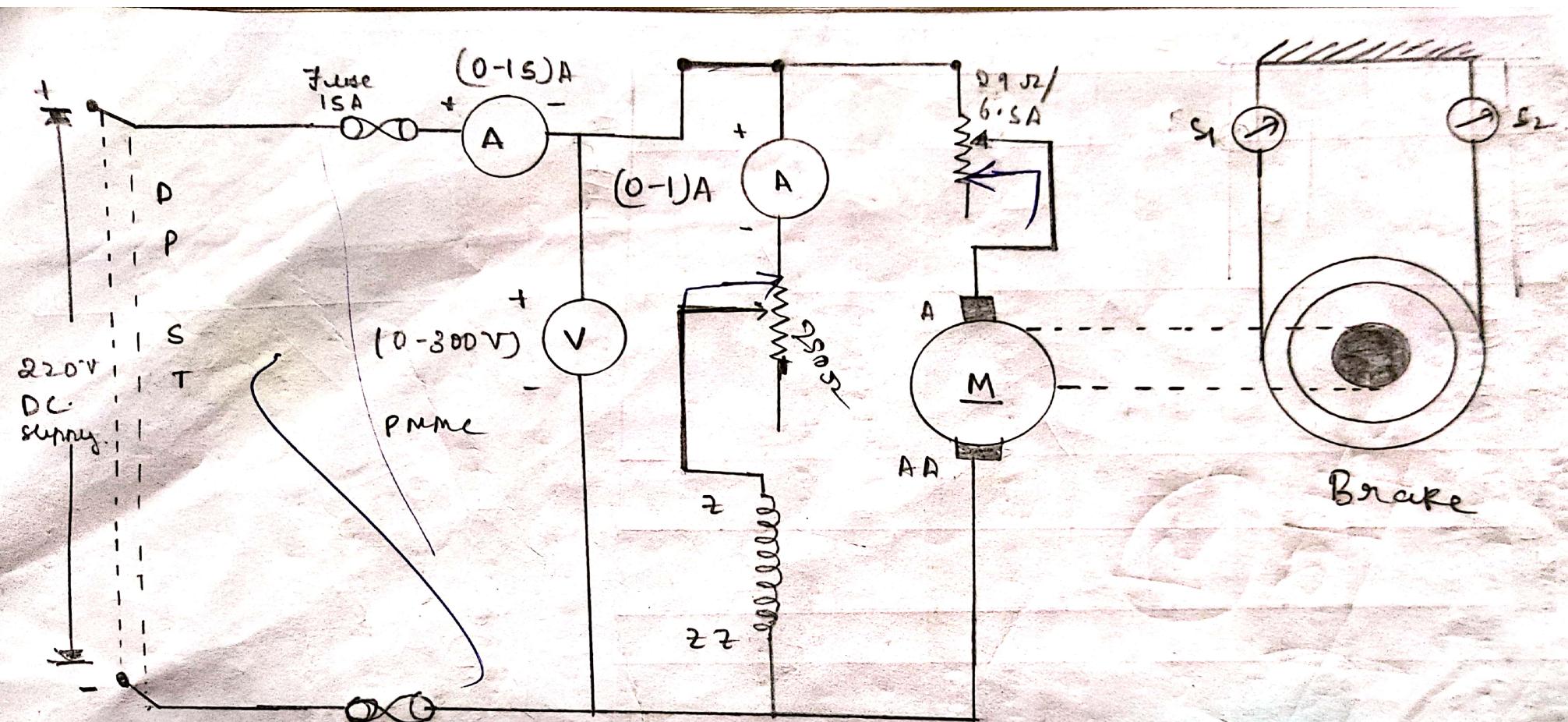

Circuit Diagram.  
 Brake test on DC shunt motor.

S.NO	Voltage (volts)	Current (A)	Current sneek (A)	Starting Balance (S <sub>1</sub> )	Game (S <sub>2</sub> )	OutPut (amt) (S <sub>3</sub> )	Final Balance (S <sub>1</sub> -S <sub>2</sub> )
1.	103 x 2 = 206	1.03 A	1560	0	0	0	23.4%
2.	104 x 2 = 208	1.03 A	1484	0	0	520	30.9%
3.	104 x 2 = 208	1.03 A	8845 A	1400	1468	1020	34.8%
4.	103 x 2 = 206	1.03 A	8845 A	1400	1455	1020	28.1%
5.	102 x 2 = 204	1.02 A	8845 A	1400	1426	1020	31.7%
6.	102 x 2 = 204	1.02 A	8845 A	1400	1446	1020	35.9%


- that the motor runs at no rated speed.
6. Note down the readings of ammeter, voltmeter and tachometer for different values of load.
  7. Continue the experiment till full load current of the motor is reached.
  8. Remove the load on the pulley and return off the pulley.
  9. Tabulate the observations and plot the required graphs.
- Precautions:
1. The motor field rheostat should be kept at minimum until one position a maximum rheostat should be at maximum position.
  2. At the time of starting, the motor should be in no load condition.
  3. Cool the pulley by using water while the experiment is performed.
  4. While measuring the radius of the pulley effective radius must be considered.
  5. Reading should be taken without hesitation
  6. Never loose connections.
- Result:  $\eta_{\text{max}} = 64\%$ ,  $T_{\text{max}} = 8.11 \text{ Nm}$
- By performing experiment on DC shunt motor the value of torque is maximum at a low value of current.

Result:-  $\eta = 64\%$ , and  $T_{max} = 8.11 \text{ Nm}$


By performing brake test on DC shunt motor efficiency is  $64\%$ , and torque of  $8.11$  is obtained.

~~22/11/16~~

### Open Circuit

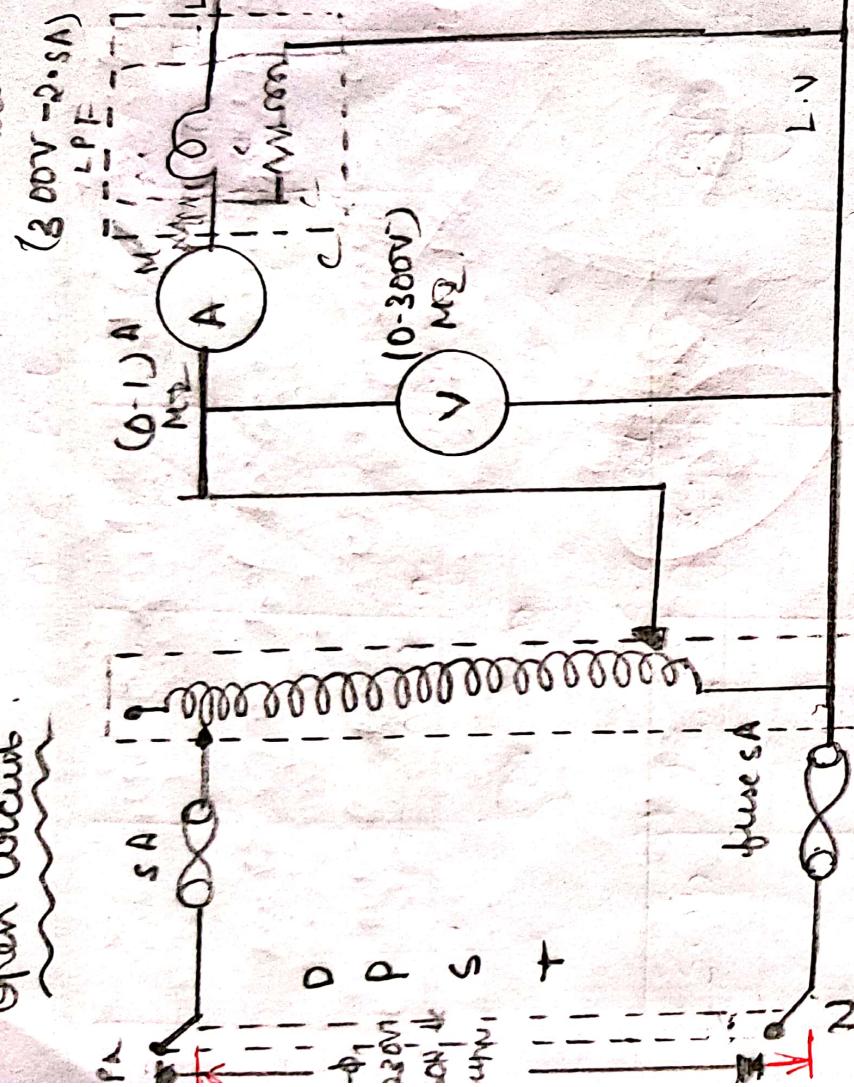

### Short Circuit

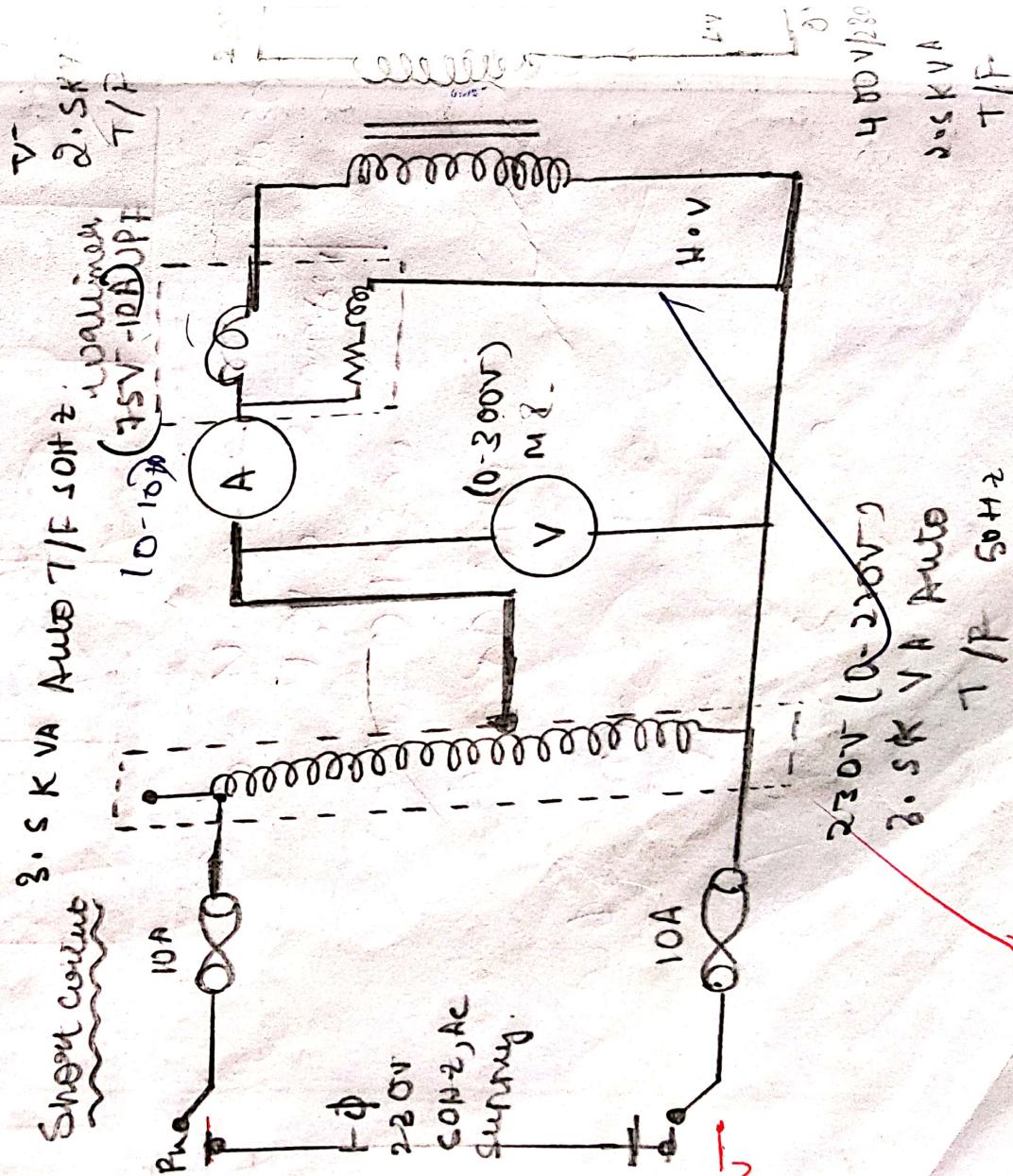

Circuit Diagram

## Experiment - V Open circuit and short circuit test on a single phase transformer

Aim: To perform open circuit and short circuit test on a single phase transformer and to find efficiency and regulation at different power factors.

### Apparatus Required:-

S.No	Apparatus	Type	Range	Quantity
1	Variac	1-Φ	1-Φ, 230V / 0-270V 50Hz	1
2	Transformer	1-Φ	Q20/400V / 12.5KV A, 50Hz	1
3	Wattmeter	LPF	300 V/2.5A	1
4	Ammeter	M2	(0-1)A	1
5	Ammeter	M1	(0-10)A	1
6	Voltmeter	UPF	75/10Ω	1
7	Ture	TCC	(0-10)A	1
8	Switch	DSPT	(0-30)A	1
9	Voltmeter	M2	0-300V 0-75V	1
10	Connecting wires			Required

### Procedure:- Open Circuit Test :

1. Connect the apparatus as per the circuit diagram
2. Apply the rated voltage to L.V windings using an auto - transformer.
3. Note down the readings of ammeter, voltmeter and wattmeter.

(10)

$\cos\phi$	fraction load ( $x$ )	load current	Opposite	from losses	Cu losses	Total losses (W)	%.
		$x^2 \times 28$	$x^2 \text{ kVA} \times \frac{1}{\cos\phi}$				
	$1/4$	$1/4 \times 625$ $= 156.25$	$1/4 \times 2500$ $= 312.5$	6	$\frac{1}{16} \times 10$ $= 6.25$	$6 + 6.25 = 12.625$	96.04%
0.5	$1/2$	$1/2 \times 6.25$ $= 3.125$	$1/2 \times 2500$ $\times 0.5 = 6.25$	6	$(\frac{1}{2})^2 \times 10$ $= 2.5$	$6 + 2.5 = 8.5$	94.91%
	$3/4$	$3/4 \times 6.25$ $= 4.6875$	$3/4 \times 2500$ $= 937.5$	6	$(\frac{3}{4})^2 \times 10$ $= 61.875$	$6 + 61.875 = 67.875$	93.24%
	1	$1 \times 6.25$ $= 6.25$	$1 \times 2500$ $= 1250$	6	$(1)^2 \times 10$ $= 110$	$6 + 110 = 116$	91.50%

Calculation:-

$$\eta = \frac{\text{O/P}}{\text{Q. P+losses}} = \frac{312.5}{312.5 + 12.625} \times 100 = 0.96043 \times 100 = 96.043\%$$

~~$$\eta = \frac{625}{625 + 33.5} \times 100 = 0.94912 \times 100 = 94.912\%$$~~

~~$$\eta = \frac{937.5}{937.5 + 67.875} \times 100 = 0.93248 \times 100 = 93.248\%$$~~

~~$$\eta = \frac{1280}{1280 + 116} \times 100 = 0.9180 \times 100 = 91.508\%$$~~

Formulas :-

$$w_0 = V_0 * Z_0 * \cos\phi_0$$

$$\cos\phi = w_0 / (V_0 * Z_0)$$

$$w_{sc} = P_{sc}^2 + R_{02}$$

$$R_{02} = w_{sc} / P_{sc}^2$$

$$Z_{02} = V_{sc} / P_{sc}$$

$$X_{02}^2 = Z_{02}^2 - R_{02}^2$$

$$\text{Voltage Regulation} = P_{sc} + (R_{02} * \cos\phi_2 + X_{02} * \sin\phi) / V_{01}$$

S.C test :-  $w_{sc} = \sqrt{P_{sc} * Z_{sc} * (R_{02})_{sc}}$

$$R_{02} = \frac{w_{sc}}{P_{sc}} = \frac{110}{6.25 \times 6.25} \quad R_{02} = 2.816 \Omega$$

$$Z_{02} = \frac{V_{sc}}{P_{sc}} = \frac{29}{6.25} = 4.64 \Omega$$

$$X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{29^2 - 4.64^2} = 21.529 \quad X_{02} = 4.029 \Omega$$

$$\% \text{ Reg} = \frac{6.25 ((2.816)(0.3) + (3.6877)(0.95)) \times 100}{29} = 93.70\%$$

~~$$\text{load} = \frac{6.25 ((2.816)(0.3) - (3.6877)(0.95))}{29} = 57.29 \Omega$$~~

O.C test :-  $\cos\phi_2 = 0.5, \sin\phi_2 = 0.866$

$$\text{Reg \% R} = \frac{6.25 ((2.816)(0.5) + (3.6877)(0.866)) \times 100}{29} = 99.159\%$$

~~$$\text{load \% R} = \frac{6.25 ((2.816)(0.5) - (3.6877)(0.866)) \times 100}{29} = 38.046\%$$~~

O.C test:

S.NO	$V_o$ (Volts)	$I_o$ (Amperes)	W <sub>o</sub> (newton)	$\cos\phi_o$	$\phi_o$
1	230	0.64	68.4 = 24	0.16304	8006480 1.407

$$\text{Cal: } \cos\phi_o = \frac{W_o}{V_o I_o} = \frac{24}{230 \times 0.64} = 0.16304$$

$$\cos\phi_o = 0.16304$$

$$\phi_o = 8006480 \quad 1.407^\circ$$

S.NO	$V_{se}$ (Volts)	$I_{se}$ (Amperes)	W <sub>se</sub> (newton)	$\cos\phi_{se}$	$\phi_{se}$
1	$\frac{58}{2} = 29$	6.25	110	0.606	52.62

$$\text{Cal: } \cos\phi_{se} = \frac{W_{se}}{V_{se} I_{se}} = \frac{110}{181.25}$$

$$\phi_{se} = 52.625^\circ$$



29/3/25. (12)

and wattmeter

4. The wattmeter readings gives the value of core loss as ohmic losses are neglected.

Short circuit test :-

1. Connect the circuit as per the circuit diagram.

2. The L.V side is short circuited

3. Apply rated current to the H.V side using auto transformer (2-12) of rated voltage.

4. Note down the readings gives the value of the ohmic loss in both the windings as core loss are negligible

Observations:- 1. Tabulate the data obtained calculated the efficiency at different power factors also obtain regulation at different loads.

2. Plot the "efficiency" and "regulation" curves

Precautions:- 1. Loose connections should be avoided

2. Readings are taken without parallam error.

3. An L.P.P wattmeter is used for OC test.



4. OC test should be done on L.V side and SC test on

H.V side for convenience.

~~Result :- 1. from efficiency curve the transformer obtains highest efficiency~~

~~Result :- 100% regulation for load = 93.70%~~

~~Voltage regulation for lag - 99.159%~~

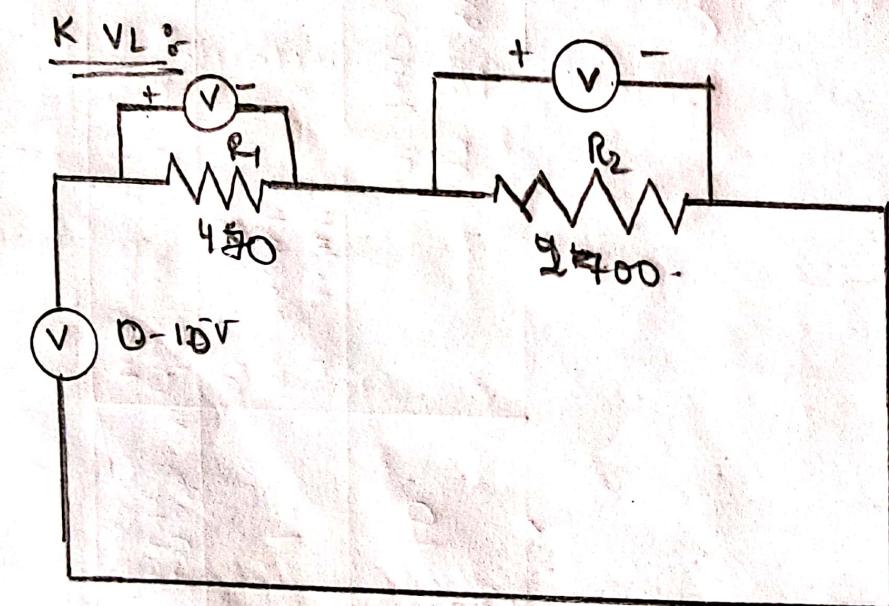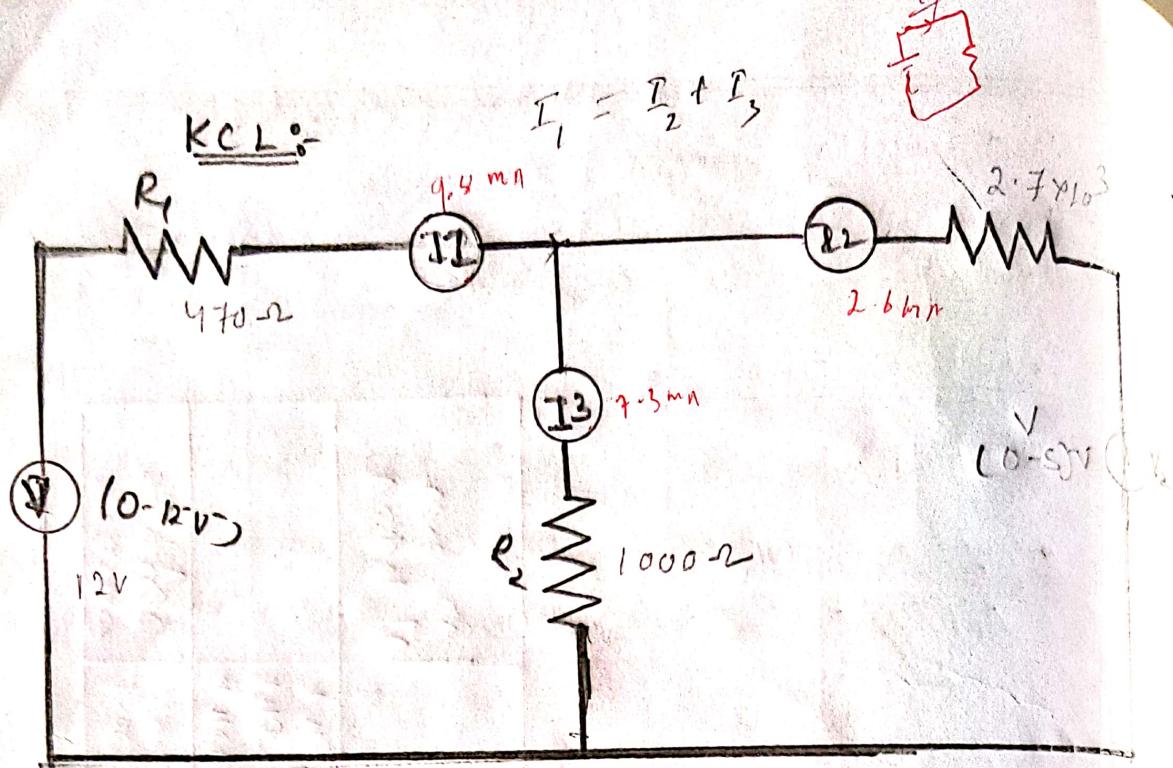

## Kirchhoff's law Experiment - VI

Aim:- To verify the Kirchhoff's voltage law and Kirchhoff's current law for the given circuit

Apparatus:- 1. Physitechs Kirchhoff's law trainer kit.  
2. voltmeter  
3. Ammeter  
4. connecting wires

Procedure:- (a) :- Kirchhoff's voltage law:

1. Connect the circuit as shown in fig.
2. measure the voltages across the resistors
3. observe that the algebraic sum of voltages in a closed loop is zero.

(b) :- Kirchhoff's current law:

1. Connect the circuit as shown in fig.
2. measure the currents through the resistors
3. observe that the algebraic sum of the currents at a node is zero

Result:- By using  $\Sigma V_L$  and  $\Sigma I_L$  we can also verify whether our measurements are consistent with the laws. If there is a significant difference between the expected value and the measured values. It may be necessary to recheck the circuit connections or the calculations.

Current Configuration	Parallel Circuit	$R_1 = 430 \Omega$ $R_2 = 270 \Omega$ $R_3 = 10 \Omega$	$I_1 = 7.7 \text{ mA}$ $I_2 = 2.6 \text{ mA}$ $I_3 = 7.4 \text{ mA}$	Measured Voltage $V_1 = 8.8 \text{ V}$ $V_2 = 8.5 \text{ V}$	Calculated Current $I_1 = 9.048 \text{ mA}$ $I_2 = 2.8 \text{ mA}$ $I_3 = 1.8 \text{ mA}$	Calculated Voltage $V_1 = 10.48 \text{ V}$ $V_2 = 8.5 \text{ V}$	Measured Voltage <del><math>V_1 = 10.48 \text{ V}</math></del> <del><math>V_2 = 8.5 \text{ V}</math></del>
Resistor Values ( $\Omega$ )	Parallel Circuit	$R_1 = 430 \Omega$ $R_2 = 270 \Omega$ $R_3 = 10 \Omega$	$I_1 = 7.7 \text{ mA}$ $I_2 = 2.6 \text{ mA}$ $I_3 = 7.4 \text{ mA}$	$V_1 = 8.8 \text{ V}$ $V_2 = 8.5 \text{ V}$	$I_1 = 9.048 \text{ mA}$ $I_2 = 2.8 \text{ mA}$ $I_3 = 1.8 \text{ mA}$	$V_1 = 10.48 \text{ V}$ $V_2 = 8.5 \text{ V}$	<del><math>V_1 = 10.48 \text{ V}</math></del> <del><math>V_2 = 8.5 \text{ V}</math></del>
Resistor Substitution Voltage ( $V$ )	Series Current	$I_1 = 7.7 \text{ mA}$ $I_2 = 2.6 \text{ mA}$ $I_3 = 7.4 \text{ mA}$	$I_1 = 7.7 \text{ mA}$ $I_2 = 2.6 \text{ mA}$ $I_3 = 7.4 \text{ mA}$	$V_1 = 8.8 \text{ V}$ $V_2 = 8.5 \text{ V}$	$I_1 = 9.048 \text{ mA}$ $I_2 = 2.8 \text{ mA}$ $I_3 = 1.8 \text{ mA}$	$V_1 = 10.48 \text{ V}$ $V_2 = 8.5 \text{ V}$	<del><math>V_1 = 10.48 \text{ V}</math></del> <del><math>V_2 = 8.5 \text{ V}</math></del>

Calculation:-

$$KCL = A_1 = A_2 + A_3$$

$$\frac{12 - V}{470} = \frac{V - 5}{2.7 \times 10^3} + \frac{V}{1000}$$

$$\frac{12}{470} + \frac{1}{540} = \frac{V}{2.7 \times 10^3} + \frac{V}{1000} + \frac{V}{470}$$

$$\frac{1}{2700} = 3.7 \times 10^{-4}, \frac{1}{1000} = 0.001, \frac{1}{470} = 2.12 \times 10^{-3}$$
$$= 0.0033, 0.001, 0.00212.$$

$$\Rightarrow 0.0255 + 1.85 \times 10^{-3} = V(3.049 \times 10^{-3})$$

$$\Rightarrow 0.0255 + 0.00185 = V(0.00349)$$

$$V = 7.836 V$$

$$A_1 = \frac{7.836}{470} = 0.0166 A$$

$$A_2 = \frac{7.836}{2.7 \times 10^3} = 2.852 \times 10^{-3}$$

$$A_3 = \frac{7.836}{1000} = 0.007836 A$$

apply KVL :-

$$V_1 = 470 \times i_1, V_2 = 2.7 \times 10^3 \times i_2$$

$$-10 + 470 i_1 + 2.7 \times 10^3 \times i_2 = 0$$

$$3170 i_1 = 10$$

$$i_1 = \frac{10}{3170} = \frac{1}{317}, 3.15 \times 10^{-3}$$

Ans  
Second



Across the resistor 470Ω.

$$V_1 = 470 \times i_1 \\ = 470 \times 2.28 \times 10^{-3}$$

$$V_1 = 1.04805 V \\ = 2.08 \times 10^{-3} V$$

$$V_2 = 2.7 \times 10^{-3} \times 2 \\ = 2.7 \times 10^{-3} \times 3.15 \times 10^{-3} \\ V_2 = 2.7 \times 3.15 = 8.505 V.$$

Result:- Hence Kirchoff's Laws are verified  
theoretically and practically